

Wiring a Layout: Part III

A NMRA Clinic presentation for:
Three Lakes Model Railroad Club
February 27th, 2011
By Roger G Blocks, P.E.



Wiring Part III

- We begin by looking at a simple DC transformer
- Then we look at and discuss block control
- We adapt that control first as an AC railroad
- Then as a DC system and compare them
- And show that children can build such systems
- And combine AC and DC on one panel and
- We find it all works with DCC & DCS as well...




Simple DC Power Supplies

- Similar to AC with a rectifier
- Range perhaps 2 – 12 VDC
- May need to fix range if DCC
- Older units may require external Circuit Breaker
- DCC (and DCS) both require quick response to a short circuit.. See manufacturer's instructions
- Will be updated/discussed in first DCC class !



AC

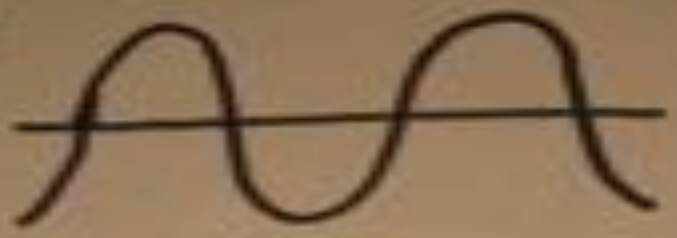


AC




COMBO -
TRANSFORMER
RECTIFIER
& THROTTLE

DC

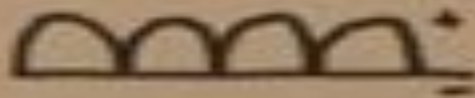


DC

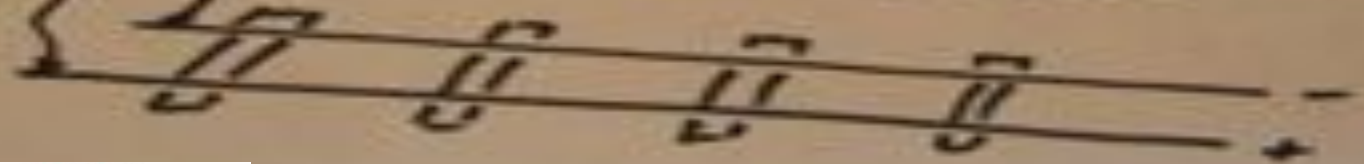

Handwritten signature



SIMPLE D.C. TRANSFORMER

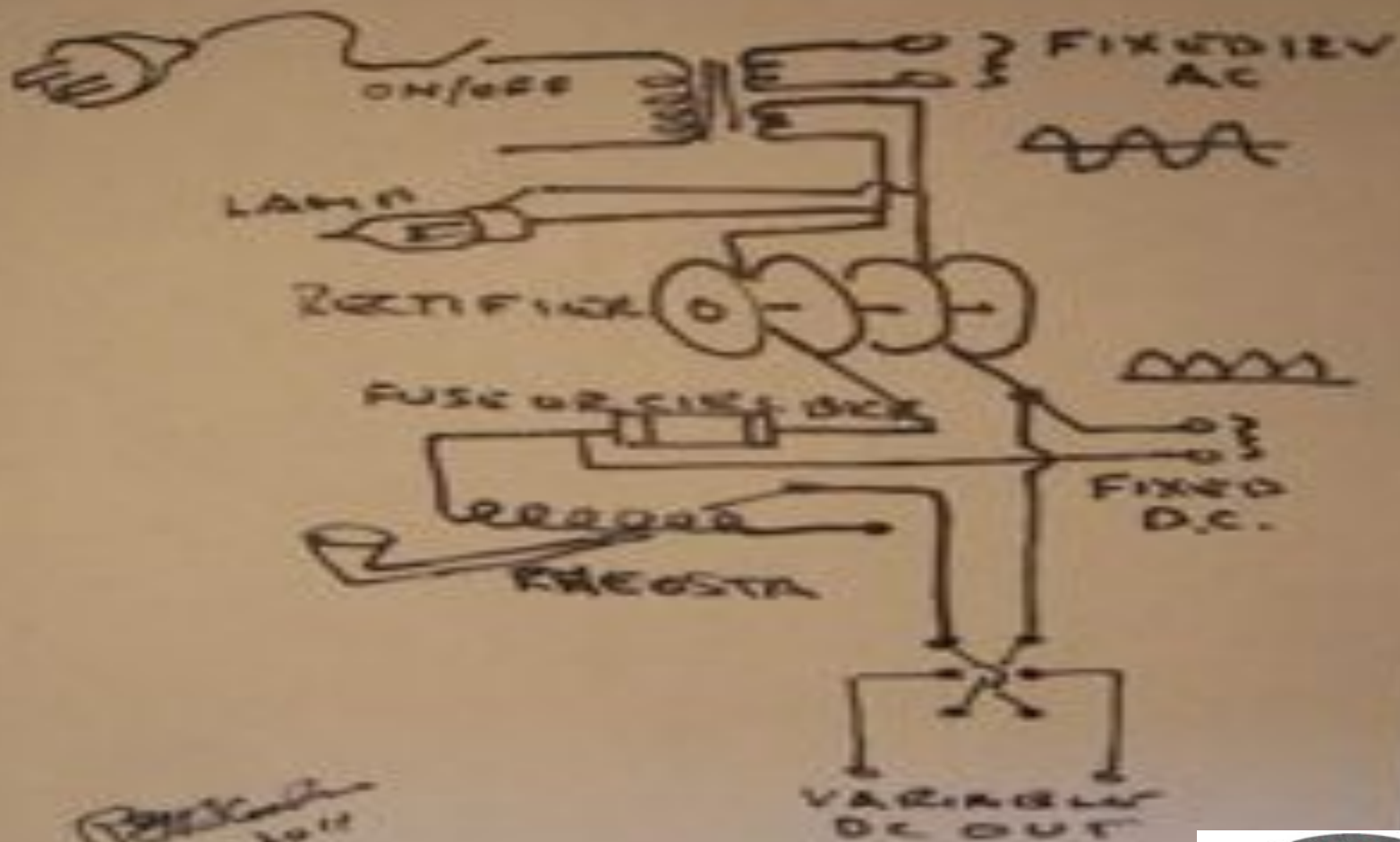

Handwritten signature
1-2017







Block Control


- A block is an electrical control zone
- Classically: more blocks = more trains
- Today's DDC, DCS & DCC: still need some
- Generally Favor: isolate both tracks
- AC three rail: signaling & accessory operation



BLOCKS

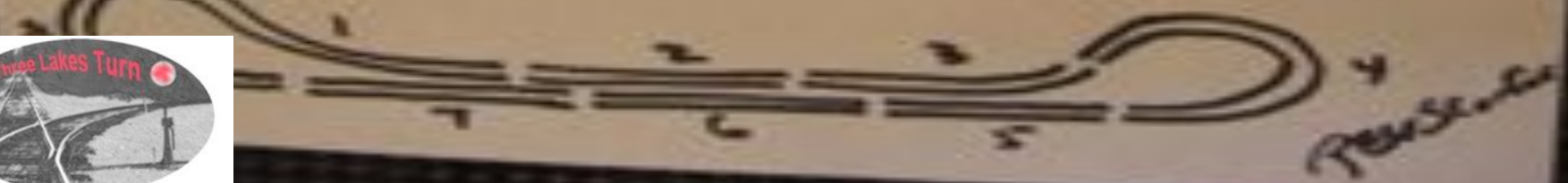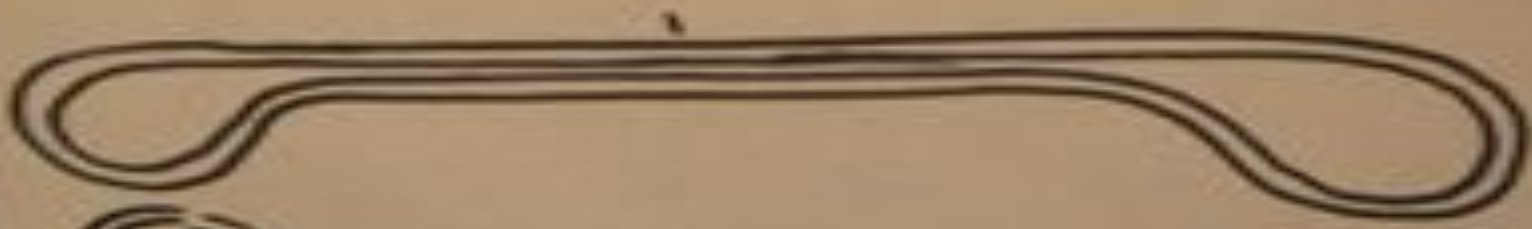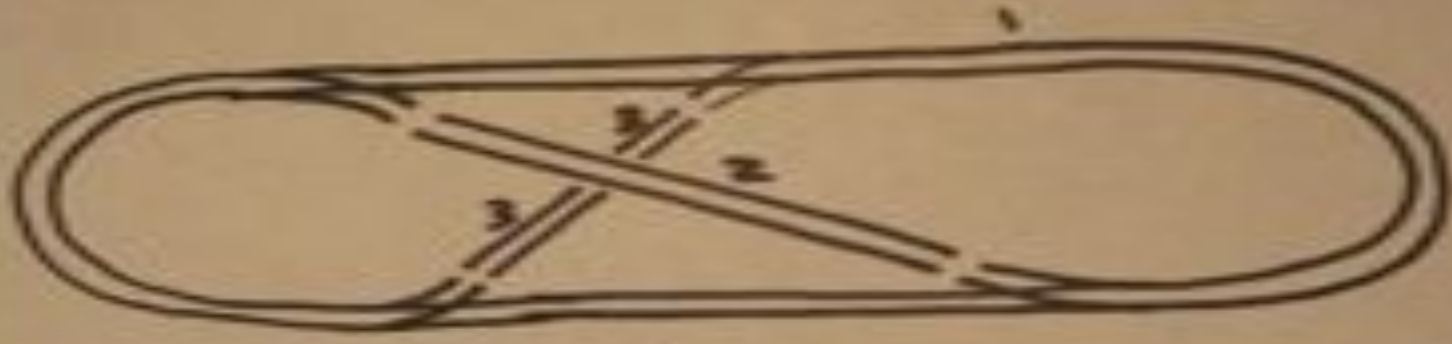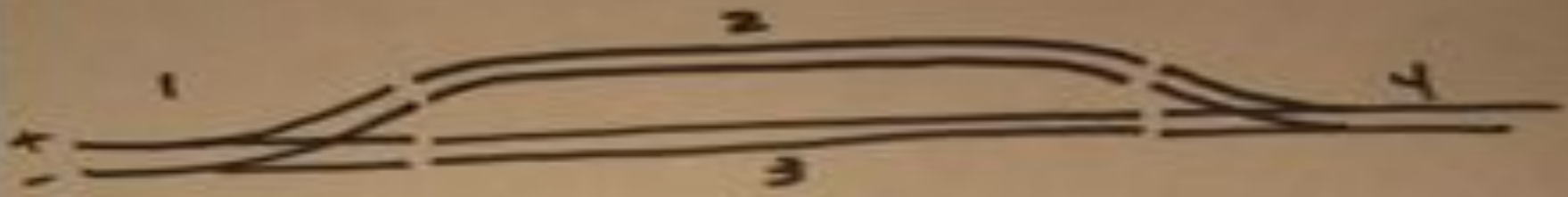


SIMPLE ON/OFF BLOCK CONTROL

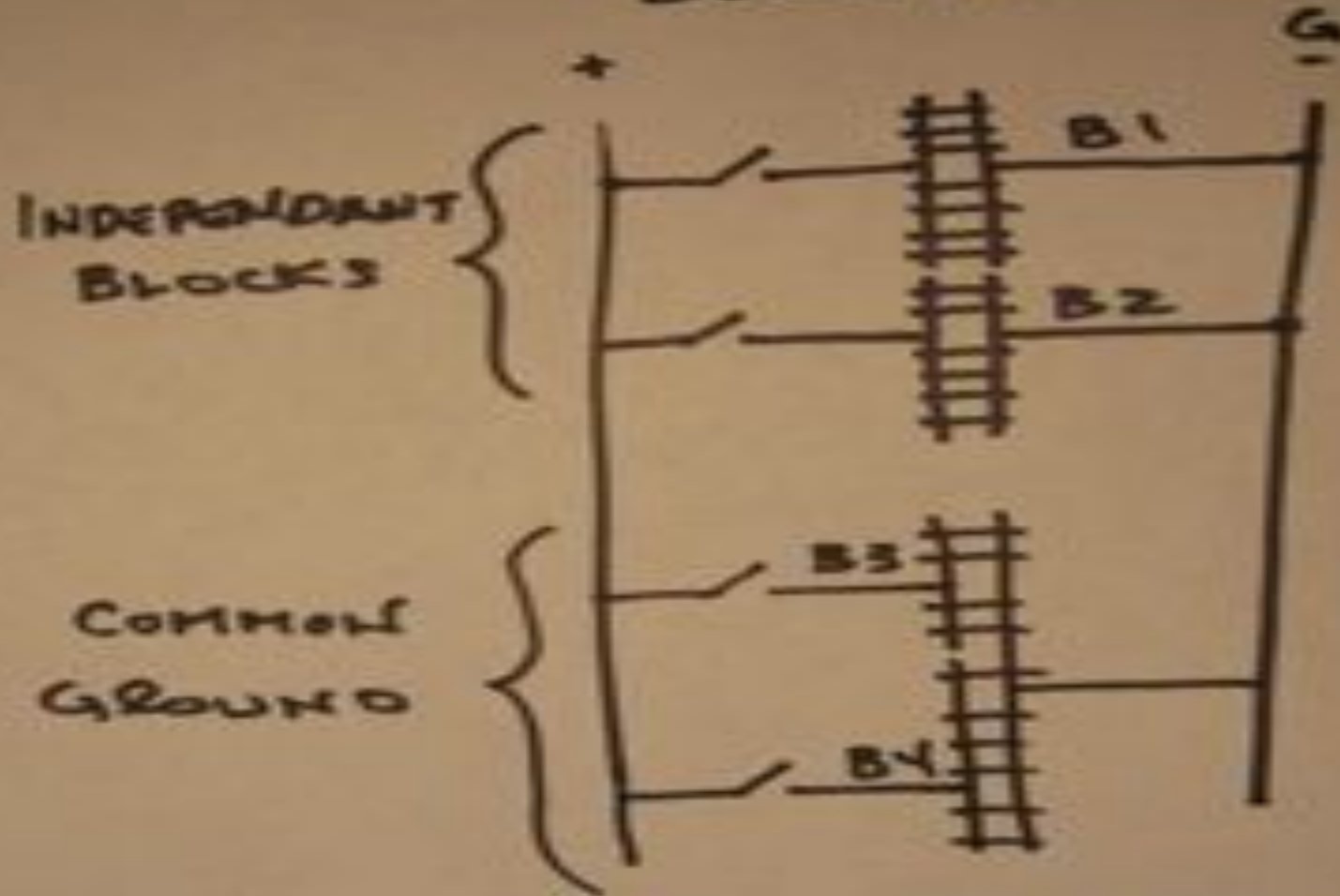

Prakash
1/2011




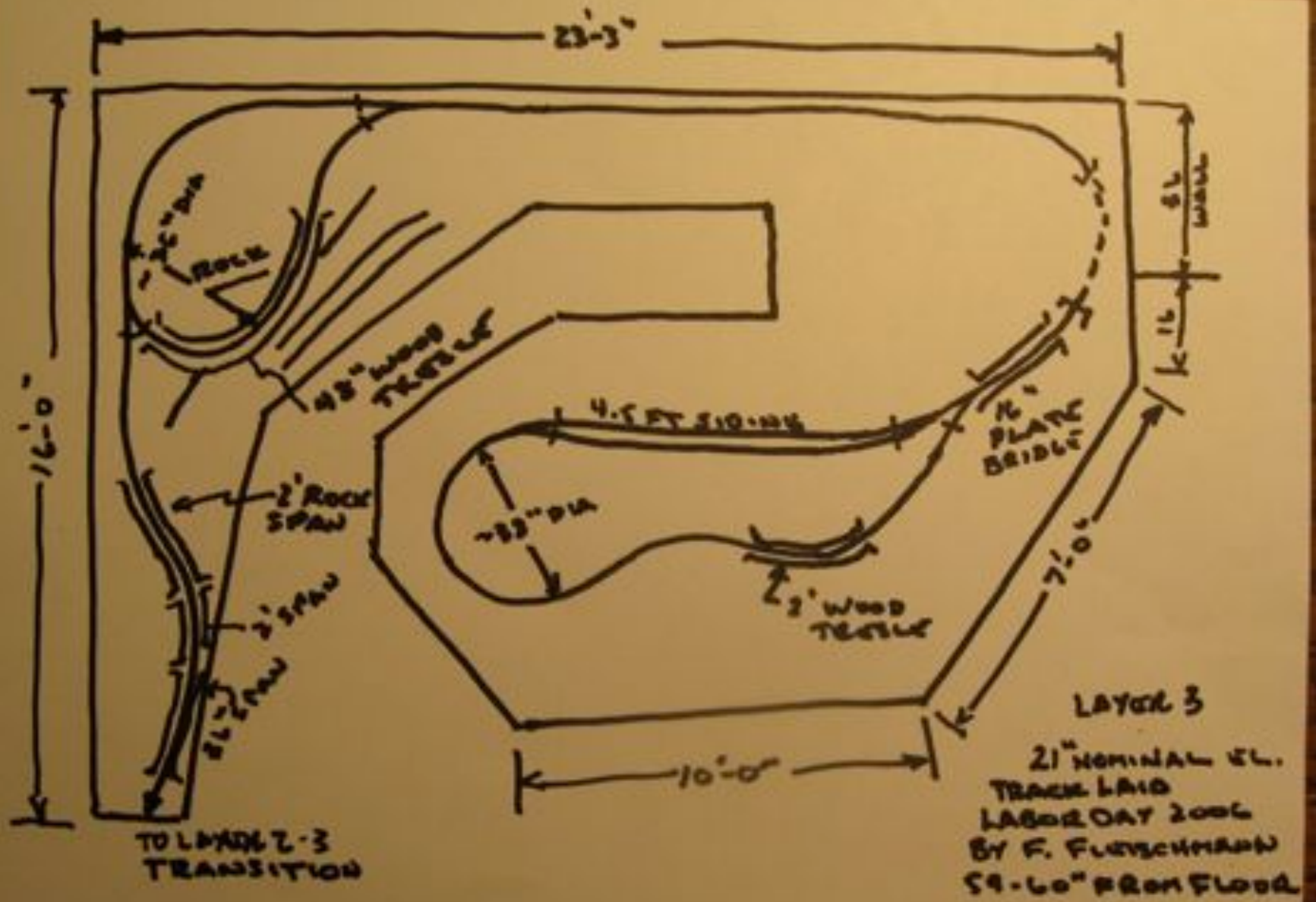

82' LAYER 3



3 RAIL A.C.

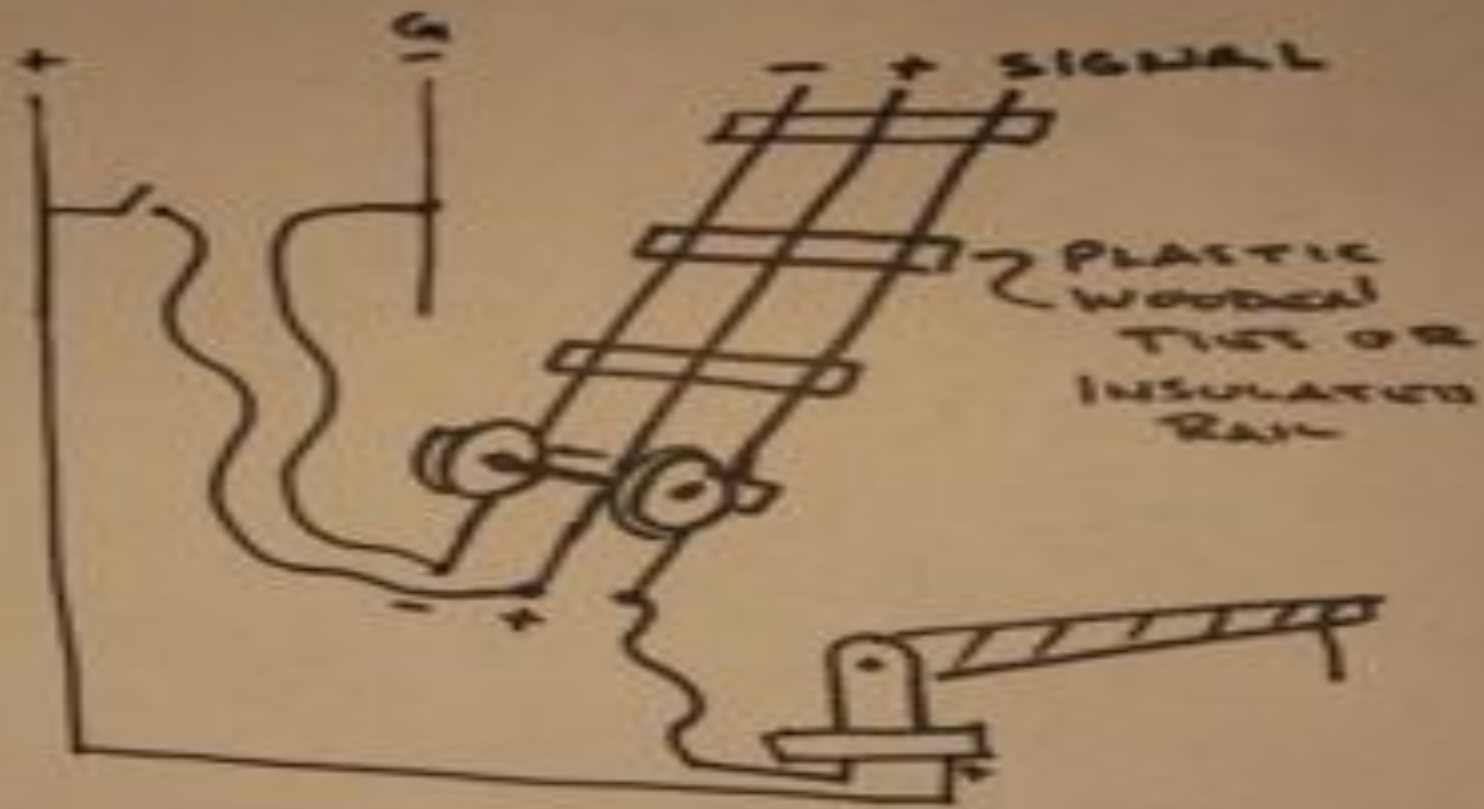

How To Use A.e.

Geoff Smith
1-2011



Reversing Engines

- Classic Lionel reversed direction in Engine
- Classic DC reversed polarity at power supply
- DCS from MTH reversed direction in Engine (AC)
- DCC now reverses direction in Engine (DC)
- Digital reversing is done via a signal on or in the power signal (a digital message)
- Want to be able to run classic DC? Keep DPDT.



REVERSING D.C.




Reverse Loops in DC

- Follow the rails, without blocks = short circuit
- Easy solution: insert a block to prevent short
- Then, add a DPDT switch to reverse polarity
- Y's, Turntables & crossovers have same challenge
- DCC for DC systems solves polarity problems at loops and crossovers with automated devices
- AC systems do not have this problem.



SIMPLE D.C. REVERSE LOOP

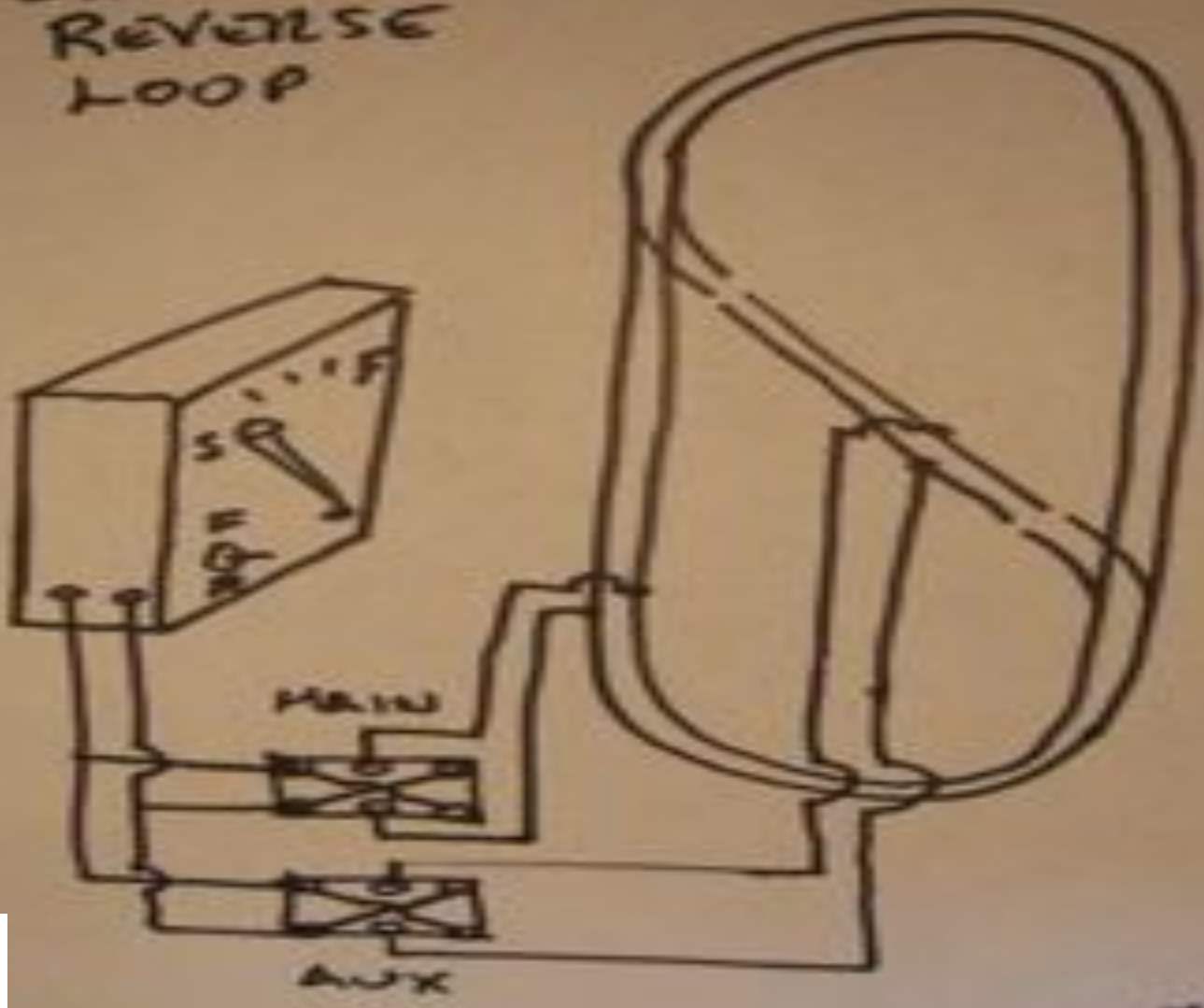

*Robert
1/2011*




Light Indication Circuits

- Indication of type and location of power
- Can be done at the same time DCS, AC or DCC
- However, you must use a DPDT or DPST switch
- Modest examples follow..



D.P. S.T.

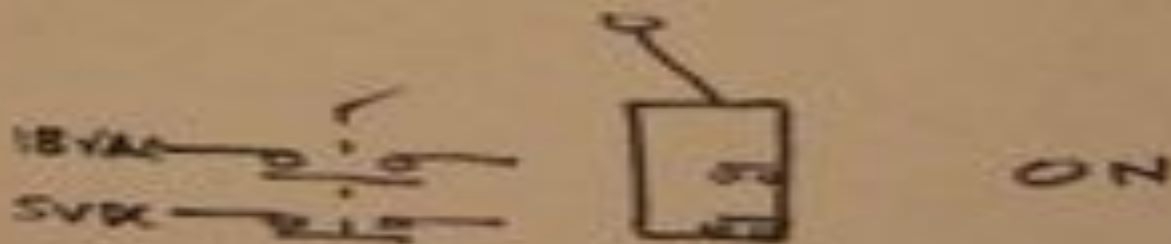


Handwritten signature
11/20/11



TRANSFER BLOCK & PROTECTIVE WIRING.

TRANSFORMER ϕ
SOURCE A 5-18VAC

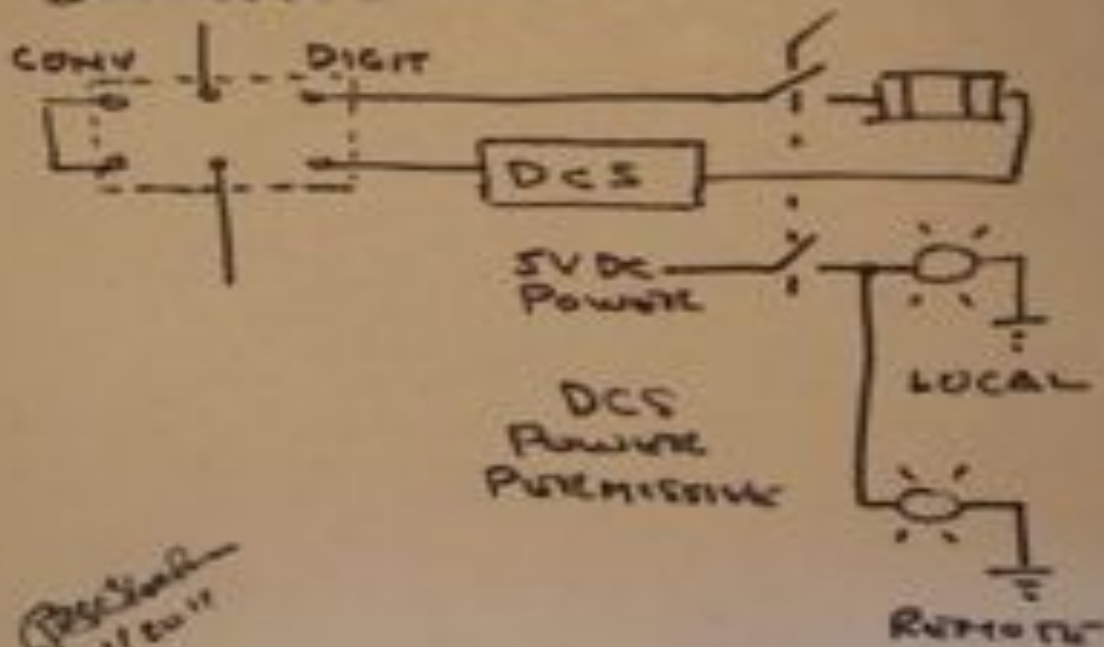








THOMASVILLE WIRING

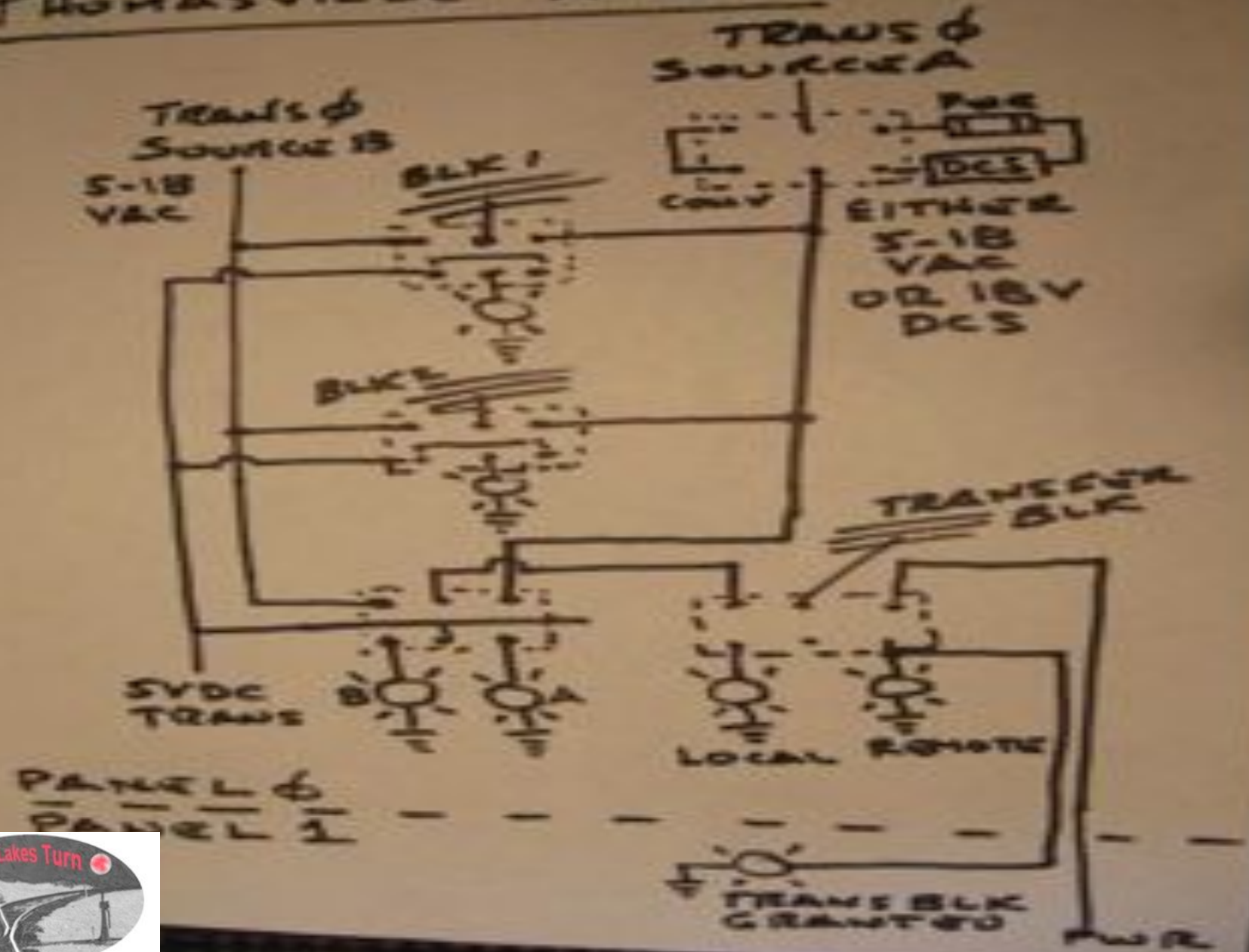





Summary

- Covered Design: Distributed vs. Centralized
- Blocks and their use
- DPDT contacts: value for reversing or two voltages
- DPST contacts: value for isolation or two voltages
- Logical design for AC and DC classic operations
- Ability to run AC / DDC / and DCS modes
- Background for Auto-Routing and DCC !





Currently wiring these details



May your life and your wiring be well planned,
without fault, clean and understandable...

This isn't the end...

Roger G Blocks, P.E.

